

(ENGLISH)

[TIME ALLOWED—3 HOURS]

(MARKS—100)

APPLIED ELECTRONICS (THEORY-II)**Marks**1. (a) Select the correct alternative and rewrite (any *five*) :—

5

(i) IC 741 is use as

(a) Timer (b) OP-AMP (c) Adder (d) Counter.

(ii) Information store in the Flip-Flop is form.

(a) Secondary (b) Analog (c) Binary (d) Primary.

(iii) multivibrator has no stable state.

(a) Monostable (b) Astable (c) Bistable (d) Multistable.

(iv) flip flop shows race condition.

(a) JK (b) RS (c) T (d) SR.

(v) Base of octal number system is

(a) 10 (b) 8 (c) 2 (d) 16.

(vi) The NAND Gate and NOR gate are also called as logic gate.

(a) Basic (b) Universal (c) Addre (d) Invertor.

(b) State *true* or *false* (any *five*) :—

5

(i) D flip-flop having one input.

(ii) Subtractor is an differential Amplifier.

(iii) Oscillator is a AC to DC convertor.

(iv) Base of Hexadecimal number system is 8.

(v) Diode is use for speed control of motor.

(vi) In Boolean algebra $A + A = 1$.(c) State long form (any *five*) :—

5

(i) LDR (ii) SISO (iii) LCD

(iv) BCD (v) OP-AMP (vi) IC.

[Turn over

- (d) Match the pair :— 5
- | | |
|------------------|-----------------|
| ‘A’ Group | ‘B’ Group |
| (i) Basic Gate | (a) $(30)_{10}$ |
| (ii) $(11110)_2$ | (b) Buffer |
| (iii) OP-AMP | (c) AND GATE |
| (iv) LED | (d) Timer |
| (v) IC 555 | (e) Display |
| | (f) $(28)_{10}$ |
2. Attempt any *two* of the following :— 16
- State De-Morgan's Theorams.
 - Draw the circuit full Adder and explain and truth table.
 - Draw and explain monostable multivibrator using IC 555 alongwith circuit diagram.
 - What is SIPO, give its appctication.
3. Answer in brief (any *two*) :— 16
- Convert following number into decimal $(11001)_2$ and $(11011)_2$.
 - Draw and explain Colppits oscillator.
 - Explain J. K. Flip-Flop and write its truth table.
 - Construct AND and NOT gate by using NAND gate only.
4. Answe in brief (any *two*):— 16
- Draw symbol and truth table of AND NOR, EX. OR, NOT gate.
 - Draw and explain inverting OP-AMP as substractor.
 - Define in detail type of number system.
 - Draw the circuit diagram of seven segment decoder and explain.
5. Write short notes (any *four*) :— 16
- Crystal oscillator.
 - LCD
 - Multiplexer
 - DC Motor
 - Photo Diode.
6. Attempt any *two* of the following :— 16
- Draw and explain Inverting OP AMP with circuit.
 - Solve.—

(i) $(1100 + 1011)$	(ii) $(1111 + 0110)$
(iii) $(11101 - 11001)$	(iv) $(10110101 - 1010110)$
 - Draw and explain square puls generator.
 - Explain about Remot Control.